

Sol: 01:

. Select the bottom node to be ground.

$$4 = 2V_x + \frac{V}{12} + \frac{V}{6}$$

$$V_x = \frac{4}{6}V$$

$$\Rightarrow V = \frac{48}{19}$$

Sol: 02:

Select the bottom node to be ground and define the top node as V:

$$12 + 2I_0 = \frac{V}{12} + \frac{V}{6} + \frac{V}{4}$$

$$I_0 = \frac{V}{6}$$

$$\Rightarrow V = 72$$

Sol: 03:

Select the bottom node to be ground. Define the node voltages, V_0 , V_1 , and V_2 across the top from left to right. Then:

$$V_1 - V_2 = 4I_0$$

$$4 = \frac{V_1}{2} + \frac{V_1}{2} + \frac{V_2}{4}$$

$$I_0 = \frac{V_1}{2}$$

$$V_0 = 8/3$$

Sol: 04:

Select the bottom node to be ground. Define the node voltages, V_1 , V_2 , and V_3 across the top from left to right. Then:

$$V_1 = 12$$

$$V_2 - V_3 = 2V_a$$

$$0 = \frac{V_2 - V_1}{2} + \frac{V_2}{4} + \frac{V_3}{6}$$

$$V_a = V_1 - V_2$$

$$\Rightarrow V_0 = V_3 = 0$$

Sol: 05:

At Node-a applying KCL:

$$\frac{V_a - 5}{4\Omega} + \frac{V_a + 5 - V_b}{4\Omega} + \frac{V_a - V_b}{2\Omega} + \frac{V_a - 0}{4\Omega} = 0$$

$$\Rightarrow 5V_a - 3V_b = 0 \quad \text{--- (i)}$$

Applying KCL at Node-b:

$$\frac{V_b - V_a}{2} + \frac{V_b - 5 - V_a}{4} + \frac{V_b - 0}{4} = 0$$

$$\Rightarrow \frac{2V_b - 2V_a + V_b - 5 - V_a + V_b}{4} = 0$$

$$\Rightarrow 4V_b - 3V_a = 5$$

$$\Rightarrow 3V_a - 4V_b = -5 \quad \text{--- (ii)}$$

Solving (i) & (ii) $\Rightarrow V_a = \frac{15}{11} = 1.36 \text{ V}$

$$\text{or } V_b = \frac{25}{11} = 2.27 \text{ V}$$

Q

Sol: 06:

Define the mesh current I_1 going counter clockwise around the right loop and I_2 going clockwise around the left loop. Then:

$$I_1 = 2$$

$$-12 + 4(I_2 + I_1) + 6 + 2I_2 = 0$$


$$\Rightarrow I_2 = -\frac{1}{3}, V_0 = -2I_2 = \frac{2}{3}$$

Sol: 07:

Ques: 07

$$I_1 + I_1 + 2I_2 + I_3 = 0$$
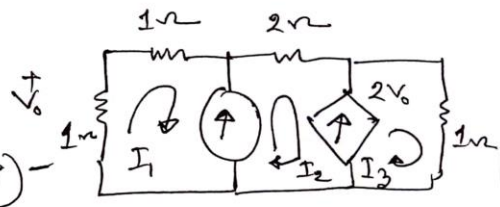
$$\Rightarrow 2I_1 + 2I_2 + I_3 = 0 \quad \text{--- e.i.)}$$



$$I_2 - I_1 = 4 \quad \text{--- e.ii.)}$$

$$I_3 - I_2 = 2V_0 \quad \text{--- e.iii.)}$$

Now, $V_0 = 1I_1$

From equation e.iii.) \Rightarrow

$$I_3 - I_2 = 2I_1$$

$$\Rightarrow 2I_1 + I_2 - I_3 = 0 \quad \text{--- e.iv.)}$$


Solving (i), (ii) and (iv)

$$I_1 = -\frac{12}{7} \text{ A} = V_0$$

$$I_2 = 16/7 \text{ A}$$

$$I_3 = -8/7 \text{ A}$$

Sol: 08:

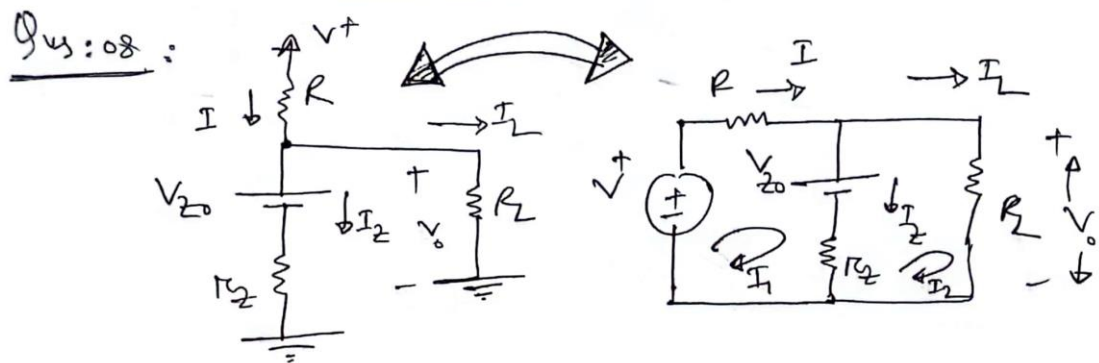

$$R = 100 \Omega, R_2 = 10 \text{ k}\Omega, R_2 = 20 \Omega, V_{20} = 3 \text{ V} \Rightarrow I_2 = 1 \text{ mA}$$

At Loop 1: $R I_1 + V_{20} + R_2 I_2 - V^+ = 0$

$$\Rightarrow 100 \times I + 3 + (20 \times 1 \times 10^{-3}) = V^+ \quad \text{--- (i)}$$

Again, $I_1 - I_2 = I_2$

$$\Rightarrow I - I_2 = 1 \text{ mA} \quad \text{--- (ii)}$$

At Loop 2: $I_2 R_2 - R_2 I_2 - V_{20} = 0$

$$\Rightarrow 10 \times 10^3 I_2 - (20 \times 10^{-3}) = 3 \quad \text{--- (iii)}$$

$$\Rightarrow I_2 = \frac{3 + 20 \times 10^{-3}}{10 \times 10^3} = 302 \mu\text{A} = 0.302 \text{ mA}$$

$$\boxed{\therefore I_2 = 0.302 \text{ mA}}$$


from (ii), $I_1 = (1 \times 10^{-3}) + I_2 = (10^{-3}) + (0.302 \times 10^{-3})$

$$\boxed{I = 1.302 \text{ mA}}$$

from (i), $\boxed{V^+ = 3.15 \text{ V}} \quad \Rightarrow \quad \boxed{V_0 = R_2 I_2 = 3.02 \text{ V}}$

Sol: 09:

Website : ieee-ictp.buet.ac.bd

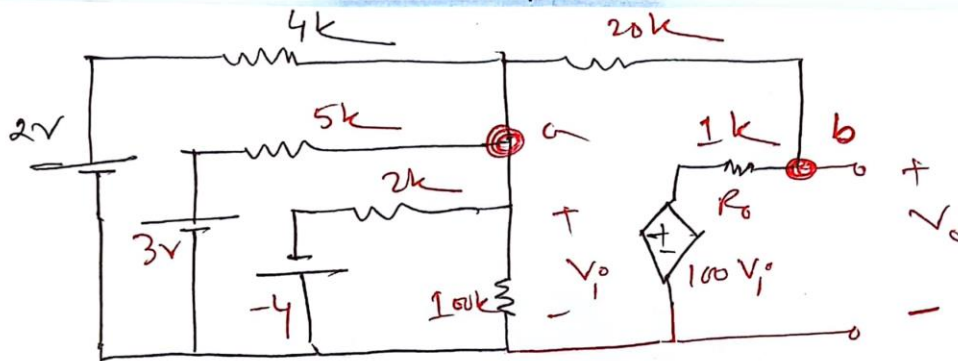

At Node a:

$$\frac{V_a - 2}{4} + \frac{V_a - 3}{5} + \frac{V_a + 4}{2} + \frac{V_a}{100} + \frac{V_a - V_b}{20} = 0 \quad \text{--- (i)}$$

At Node b:

$$\frac{V_b - V_a}{20} + \frac{V_b - 100V_1}{1} = 0$$


$$\Rightarrow \frac{V_b - V_a}{20} + \frac{V_b - 100V_a}{1} = 0 \quad \text{--- (ii)}$$

Solve (i) & (ii) \Rightarrow


$V_a = \text{calculate}$

$V_b = \text{calculate}$

Sol: 10:

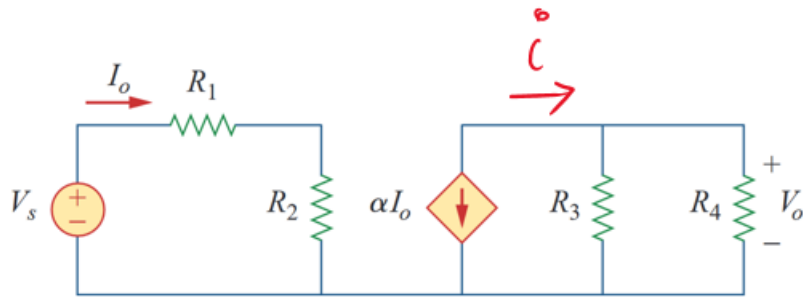

Sol: 11:

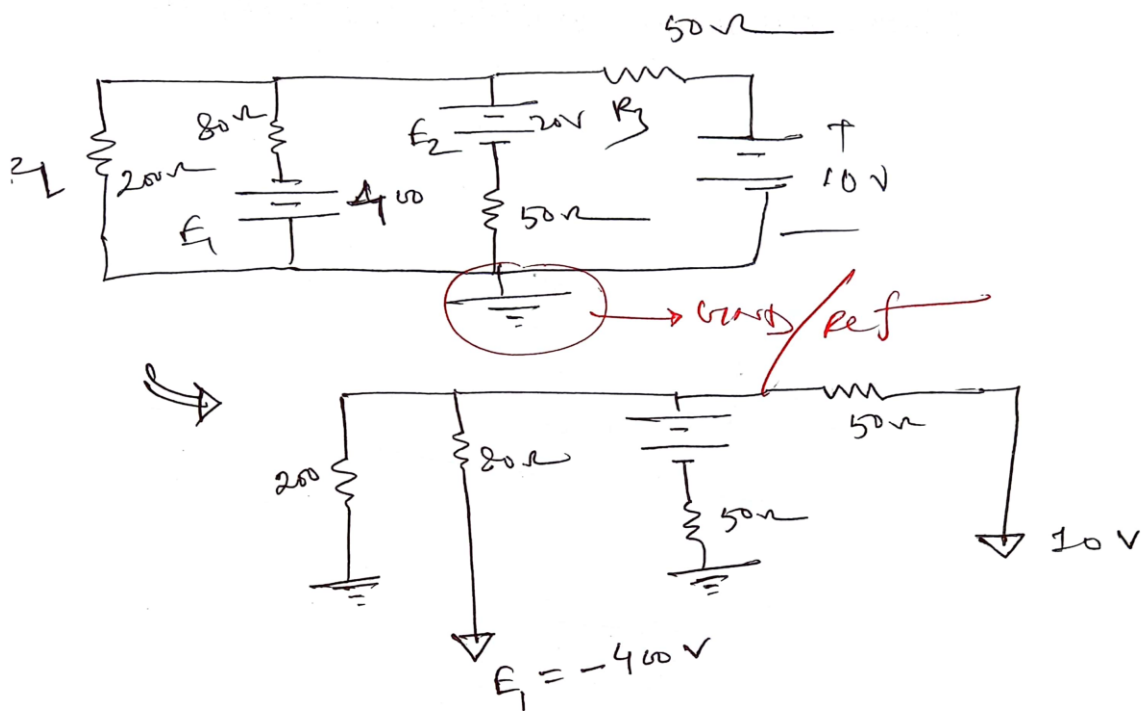

Sol: 12:

Question 12: (i) $V_0 = 3V$ and $R = 3 \left[\frac{1}{R} = m \right]$

