

**BRAC University**  
**Semester: Fall 2024, Faculty: YAP**  
**Course: CSE 251**

<b>Assignment: 03</b>	<b>Deadline: 04 Jan., 2025 (11:59 PM)</b>	<b>Marks: 90</b>
-----------------------	---	------------------

**Instruction:**

- Clearly write the solutions, along with the questions, on white paper with black ink (no need to use color pen, don't use pencils).
- Use CamScanner, Adobe Scan, Microsoft Office Lens, or any other software to scan the pages and make a single PDF file.
- After creating the PDF, make sure that (a) no pages are missing, (b) all of the pages are legible, and (c) your student ID on each page is visible.
- Please note, collaboration  $\neq$  copying. You are allowed to discuss the questions and clear confusion you might have, but you have to write your solutions independently and be able to explain your answers during a random viva.
- [Very Important] Rename the PDF in the following format: "Section A4 StudentID FullNameWithoutSpace.pdf". For example, if my student ID is 12345678 and my name is Yeasin Arafat, the filename should be A4 12345678 YeasinArafat.pdf .

■ **Question 1 of 8** [CO3] [10 marks]


Refer to the MOSFET in the figure below where  $V_T = 1\text{ V}$  and  $K = k_n' W/L = 4\text{ mA/V}^2$  – for questions (a-c).

(a) [CO1] Identify the value of the gate voltage  $V_G$  and the drain-source current  $i_{DS}$ . [1]

(b) [CO2] Calculate the drain voltage  $V_D$ . [2]

(c) [CO2] Analyze the circuit to find the source voltage  $V_S$ . [Use the method of assumed states.] [3]

 
(d) [CO3] Consider a MOSFET inverter (SR model) with the following circuit parameters:  $V_{CC} = 10\text{ V}$ ,  $R_L = 10\text{ k}\Omega$ . Also, for the MOSFET,  $V_T = 1\text{ V}$  and  $1/(k_n' V_{OV}) = 5$ . Determine a  $W/L$  sizing for the MOSFET so that the inverter output of logical 0 can switch OFF the next MOSFET inverter connected to it. [4]



### ■ Question 2 of 8 [10 marks]

Refer to the MOSFET circuit in the adjacent figure where  $V_T = 1\text{ V}$  and  $k_n' = 250\text{ }\mu\text{A/V}^2$   $W/L = 1/8$  for both Q1 and Q2.

 
- (a) [CO2] Assuming Triode mode of operation, find the voltage  $V_{S1}$  and  $V_B$ . [5]
- (b) [CO2] Calculate the current  $I_{D1}$ . [2]
- (c) [CO2] Use the value of  $V_B$  obtained in (a) to find the value of resistor  $R$  so that  $V_O = -1\text{ V}$ . [3]



### Question 3 of 8 [10 marks]


Refer to the BJT circuit in the adjacent figure where,  $V_{BB} = 5\text{ V}$ ,  $V_{CC} = 15\text{ V}$ ,  $4R_1 = R_2 = 40R_3 = 80R_4 = 80\text{ k}\Omega$ . Also, assume that the common emitter current gain  $\beta = 100$ .

 - (a) [CO1] Draw the equivalent circuit of an npn-BJT during active mode. [2]
- (b) [CO2] Calculate  $I_B$ ,  $I_C$ ,  $I_E$ ,  $V_{CE}$  and  $V_C$  using the method of assumed states. [Hint: Try to find the Thevenin's equivalent circuit of the left hand side circuit from the B terminal and ground] [3]
- (c) [CO2] If  $V_{BB}$  is changed from 5V to 5.3V, what happens to the outputs of the circuits? Calculate  $I_B$ ,  $I_C$ ,  $I_E$ ,  $V_{CE}$  and  $V_C$  again. Now for a 0.3 V increase in input  $V_{BB}$ , what is the change of  $I_C$ ? Use  $\Delta I_C = I_{C,\text{new}} - I_{C,\text{old}}$ . [4]
- (d) [CO1] Explain any use case of the differences in voltage increase between input and output. What could the use case be to such a phenomenon? [1]




### ■ Question 4 of 8 [10 marks]

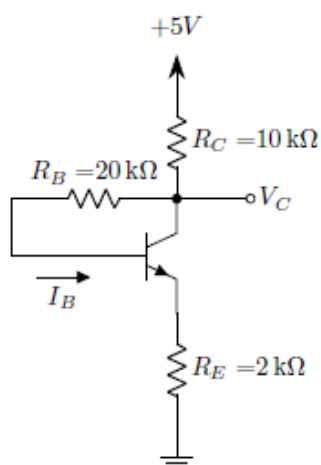- (a) [CO2] For the transistors in the figure (a) and (b) below,  $\beta = 75$ . Find the labelled voltages and [6] currents. (Assume  $v_{BE0} = 0.7\text{ V}$ , for active mode and  $v_{CE(\text{sat})} = 0.2\text{ V}$ )




(a) Circuit-1

 

(b) Circuit-2

 
- (b) [CO2] In the circuit shown in adjacent figure, the values of [4] measured parameters are shown. Determine  $\beta$ ,  $\alpha$  and the other labeled currents and voltages.



### ■ Question 5 of 8 [CO3] [10 marks]

Refer to the BJT in the adjacent figure where  $v_{BE0} = 0.7\text{ V}$ ,  $v_{CE(sat)} = 0.2\text{ V}$  and  $\beta = 100$ .

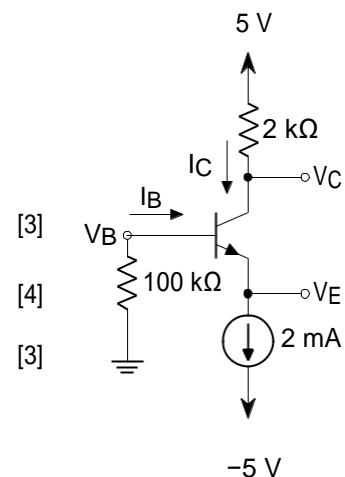- (a) [CO1] Identify the value of the BJT currents  $I_B$ ,  $I_C$  and  $I_E$ .  
 (b) [CO2] Calculate the base and collector voltages  $V_B$  and  $V_C$ .  
 (c) [CO2] Analyze the circuit to find the emitter voltage  $V_E$ . [Use the method of assumed states.]




### ■ Question 6 of 8 [10 marks]

(d)

Refer to the BJT circuit in the adjacent figure where  $v_{BE0} = 0.7\text{ V}$ ,  $v_{CE(sat)} = 0.2\text{ V}$  and  $\beta = 100$ . for both the BJTs.

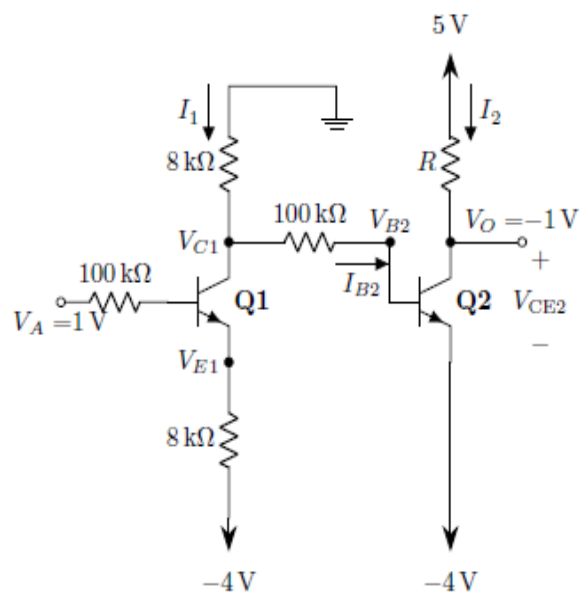
- (a) [CO2] Assuming **Saturation** mode of operation, and  $I_{B2} = 0$ , find the the voltage  $V_{C1}$  and current  $V_{E1}$ . [6]  
 (b) [CO2] Calculate the voltage value  $V_{B2}$ , so that  $V_O = -1\text{ V}$ . [Hint: Try to identify the mode of operation of Q2 with the help of  $V_{CE2}$ . Thereafter, find the value of  $V_{B2}$ .] [1]  
 (c) [C02] Find the value of resistor  $R$  so that  $V_O = -1\text{ V}$ . [1]  
 (d) [C01] Explain why the solution of the circuit, as per the above questions, is not perfectly accurate but an approximation of the true solution. State the process in which you may find the true solution. [2]



## **Question 7 of 8 [20 marks]**

 **Part 1:** The input of a full-wave rectifier is a **square wave** voltage with peak  $V_M = 15\text{ V}$  and frequency  $0.5\text{ Hz}$ , and output load resistance is  $R = 5\text{ k}\Omega$ . Silicon diodes are used in this circuit for which the forward drop is  $V_{D0} = 0.7\text{ V}$ .

- Briefly explain the purpose of a rectifier and describe its operation. [3]
- Describe the purpose of using a filter capacitor in a rectifier. [2]
- Show the input and output waveforms. [4]
- Draw the output waveforms if we add a filter capacitor,  $C = 1000\text{ }\mu\text{F}$  in parallel with  $R$ . [3]
- Draw the VTC curve [2]



(b) Input of the FW rectifier

**Part 2:** A voltage waveform  $V_i = 15 \sin(2000\pi t)\text{ V}$  is fed into a Half-wave rectifier with a load resistance  $R = 5\text{ k}\Omega$ . Silicon diodes are used in this circuit for which the forward drop is  $V_{D0} = 0.7\text{ V}$ .

- Illustrate** the input and output waveforms in separate graphs. Label the graph and **indicate** the voltage levels properly. [2]
- Calculate** the DC/Average value of the output. [1]
- A capacitor is now added to reduce the fluctuation of the output voltage, which makes the peak to peak ripple voltage **4%** of the maximum output voltage  $V_P$ . **Deduce** is the value of the capacitor from the given data. [2]
- The input of a Full-wave rectifier is shown in Figure 1(b) above and output load resistance is  $R = 10\text{ k}\Omega$ . Germanium diodes are used in this circuit for which the forward drop is  $V_{D0} = 0.3\text{ V}$ . **Show** the input and output waveforms [1]

■ **Question 8 of 8** [10 marks]

- (a) Briefly explain the operation principle of a MOSFET as a switch with appropriate illustrations showing gate bias voltage [4]
- (b) Draw the IV curve of a MOSFET considering the S-model only [2]
- (c) Design a circuit using ideal MOSFETs (S-model) and BJTs to implement the logic function:  
[1.5+1.5+1.5+1.5]

$$(1) \quad F = \overline{(\overline{A \cdot C} + \overline{\overline{A} + \overline{B}})}$$

$$(2) \quad F = \overline{(A + \overline{B}) \cdot (\overline{B} + B \cdot \overline{C})}$$